

3rd Semester B.Tech. Mid Term Examination 2021-22

DIGITAL ELECTRONICS(BTEC-T-ES-003)

Duration: 01:30

Full Marks: 25

1 Answer All

- a The minimized form of the logical expression $(A'B'C' + A'BC' + A'BC + ABC')$ is _____ . 1
- b Determine the values of A, B, C, and D that make the product term $\overline{A}B\overline{C}D$ equal to 1. 1
- c Find the complement of the expression $A'B+CD'$. 1
- d Simplify the following Boolean expression
 $F=AB+A'C+BC$ 1
- e Implement EX-NOR gate using 4:1 MUX. 1
- f Convert decimal numbers 97 and 63.4 to BCD 1

2 Answer All

- a Find $(1010)_2 - (1101)_2$ using 2's complement method 3
- b Simplify the Boolean function using K-MAP: $F = A'B'D' + A'CD + A'BC$ and $d = A'BC'D + ACD + AB'D'$, where "d" indicates Don't care conditions. 3
- c Implement $F = (A+B)(C+D)(D'+E')$ using NOR gate only 3

3 Answer any One

- a Explain how the negative numbers are represented in binary numbering systems with example. Discuss the properties of 2's complement format with example. 5
- b Minimize the following expression using Boolean Algebra and Implement it using NAND gates only. 5
 $f = A [B + C' (AB + AC')']$

4 Answer any One

- a Obtain the minimal sum of products expression for the following function and implement the same using universal gates. 5
 $f(A,B,C,D) = \sum(0, 2, 3, 5, 7, 8, 13) + \sum_d(1,6,12)$
- b Implement $F(A, B, C) = \sum_m(1, 2, 6, 7)$ using 8:1 MUX only, 4:1 MUX only, and 2:1 MUX only. 5